

Introduction to Computer Science & Engineering

Lecture 4: Gates and Circuits

Jeonghun Park

Gates and Circuits

- Gate
 - ▶ A device that operates a basic operation on electrical signals
- Circuits
 - ▶ Combined gates to perform more complicated tasks

Descriptions

- Boolean operation
 - ▶ A mathematical notation expressing two valued-logic
- Logic diagram
 - ▶ A graphical representation of a circuit;
 - ▶ Each gate has its own symbol
- Truth table
 - ▶ A table showing all possible input values and the associated output values

Gates

- Six types

- ▶ NOT

- ▶ AND

- ▶ OR

- ▶ XOR

- ▶ NAND

- ▶ NOR

NOT

- Accepts single input
- Returns the complementary signal as output

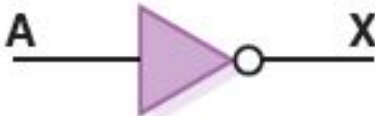
Boolean Expression	Logic Diagram Symbol	Truth Table						
$X = A'$		<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0
A	X							
0	1							
1	0							

FIGURE 4.1 Representations of a NOT gate

AND

- Accepts two inputs
- Returns 1 only if two inputs are both 1

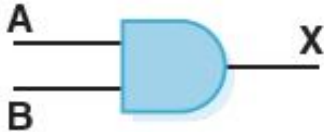
Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \cdot B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X															
0	0	0															
0	1	0															
1	0	0															
1	1	1															

FIGURE 4.2 Representations of an AND gate

OR

- Accepts two inputs
- Returns 0 only if two inputs are both 0

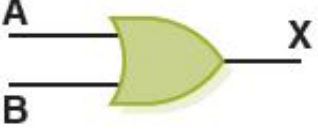
Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A + B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

FIGURE 4.3 Representations of an OR gate

XOR

- Accepts two inputs
- Returns 0 if two inputs are same
- Returns 1 if two inputs are different

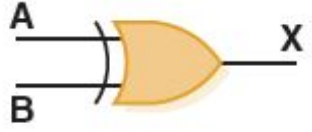
Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \oplus B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

FIGURE 4.4 Representations of an XOR gate

Some Notes

- Note the difference between the **XOR** gate and the **OR** gate; they differ only in one input situation
 - ▶ When both input signals are 1, the OR gate produces a 1 and the XOR produces a 0
- XOR is called the *exclusive OR* because its output is 1 if (and only if):
 - ▶ *either* one input *or* the other is 1,
 - ▶ *excluding* the case that they both are

NAND

- Accepts two inputs
- Returns 0 only if two inputs are both 1

 


FIGURE 4.5 Representations of a NAND gate

NOR

- Accepts two inputs
- Returns 1 only if two inputs are both 0


Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A + B)'$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															

FIGURE 4.6 Representations of a NOR gate

Gates with More Inputs

- Some gates can be generalized to accept three or more input values

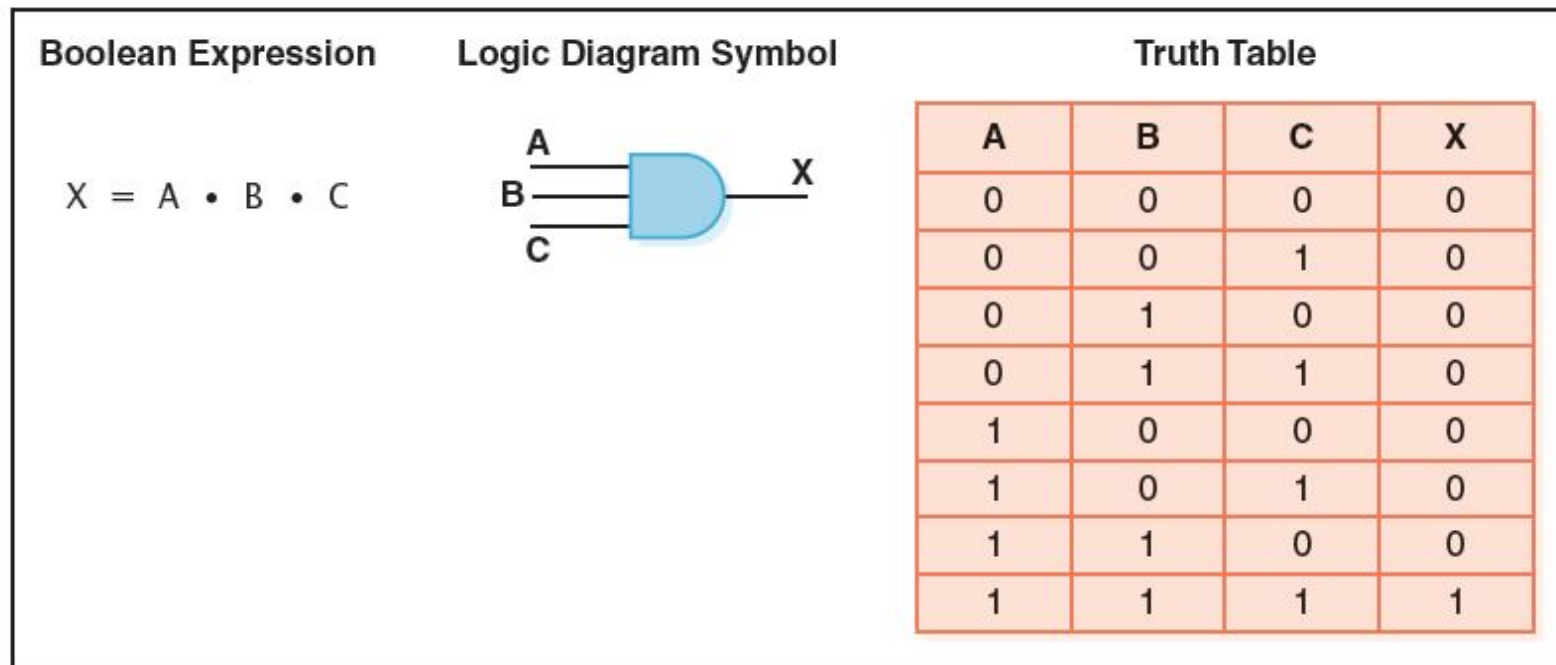


FIGURE 4.7 Representations of a three-input AND gate

Constructing Gates

- Transistor
 - ▶ A device that acts either as a wire that conducts electricity or as a resistor that blocks the flow of electricity, depending on the voltage level of an input signal
 - ▶ A transistor has no moving parts, yet acts like a switch
 - ▶ It is made of a semiconductor material, which is neither a particularly good conductor of electricity nor a particularly good insulator

NOT Gate Example

- If the Base signal is low, the transistor acts like an open switch, so the output is same as the source
- If the Base signal is high, the transistor acts like an closed switch, so the Output is pulled low


 


FIGURE 4.8 The connections of a transistor

More Examples

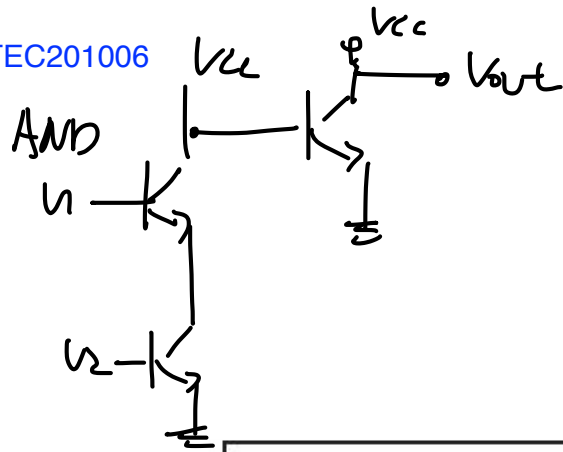





NOT gate	NAND gate	NOR gate
		



FIGURE 4.9 Constructing gates using transistors

Circuits

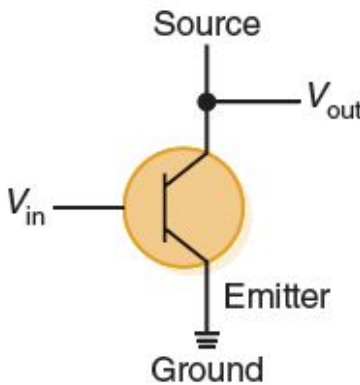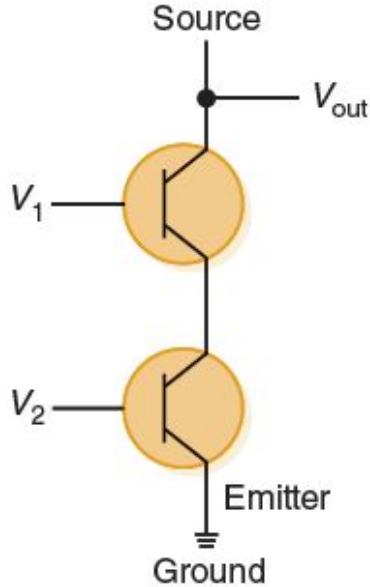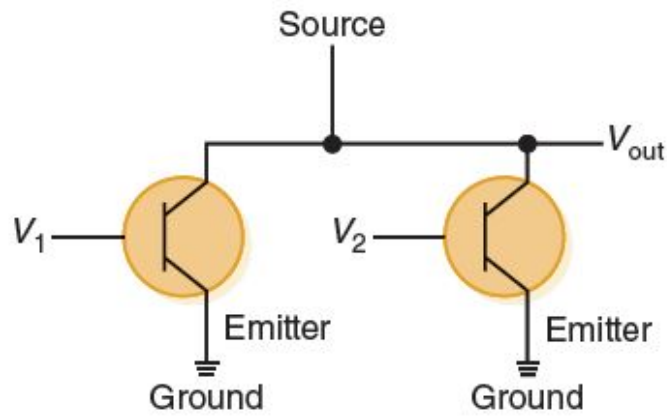 - Gates are combined into circuits by using the output of one gate as the input for another




Truth Table

  

A	B	C	D	E	X
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

Circuits

 

A	B	C	$B + C$	$A(B + C)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Different One?

Circuits


- Two example circuits are equivalent
- Boolean algebra
 - ▶ Distributive law is satisfied in Boolean algebra
 - ▶ $AB + AC = A(B+C)$

Other Properties

PROPERTY	AND	OR
Commutative	$AB = BA$	$A + B = B + A$
Associative	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive	$A(B + C) = (AB) + (AC)$	$A + (BC) = (A + B)(A + C)$
Identity	$A1 = A$	$A + 0 = A$
Complement	$A(A') = 0$	$A + (A') = 1$
De Morgan's law	$(AB)' = A' \text{ OR } B'$	$(A + B)' = A'B'$

Adders

- How we implement the addition in binary with the gates?
- Two things we care:
 - ▶ Sum
 - ▶ Carry




A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Implementation


- Boolean expression

- ▶ $\text{Sum} = A \oplus B$

- ▶ $\text{Carry} = AB$

 

Full Adders

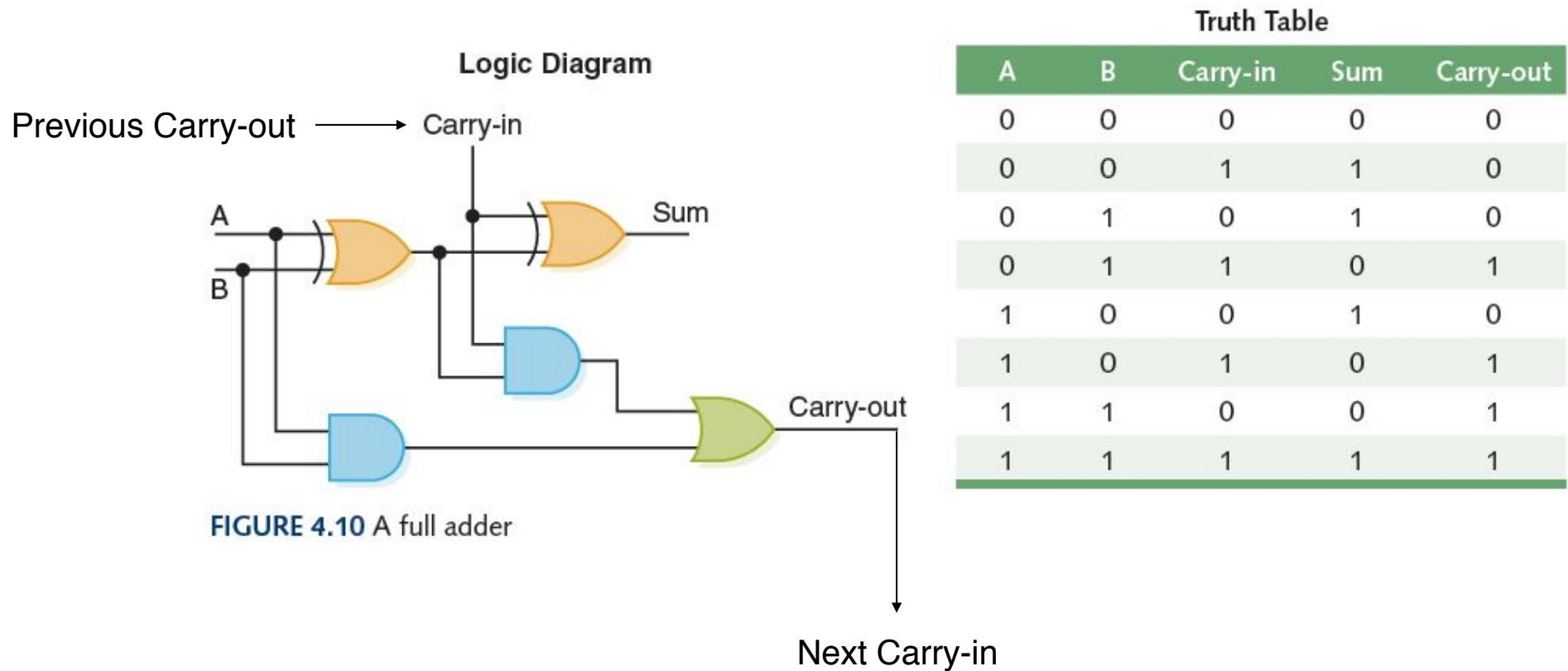

Multiplexers

- The control lines S0, S1, and S2 determine which of eight other input lines (D0 ... D7) are routed to the output (F)

S0	S1	S2	F
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

 


FIGURE 4.11 A block diagram of a multiplexer with three select control lines

Circuits as Memory

- Digital circuits can be used to store information
- These circuits form a sequential circuit, because the output of the circuit is also used as input to the circuit

S-R Latch

- SR Latch with NAND gates

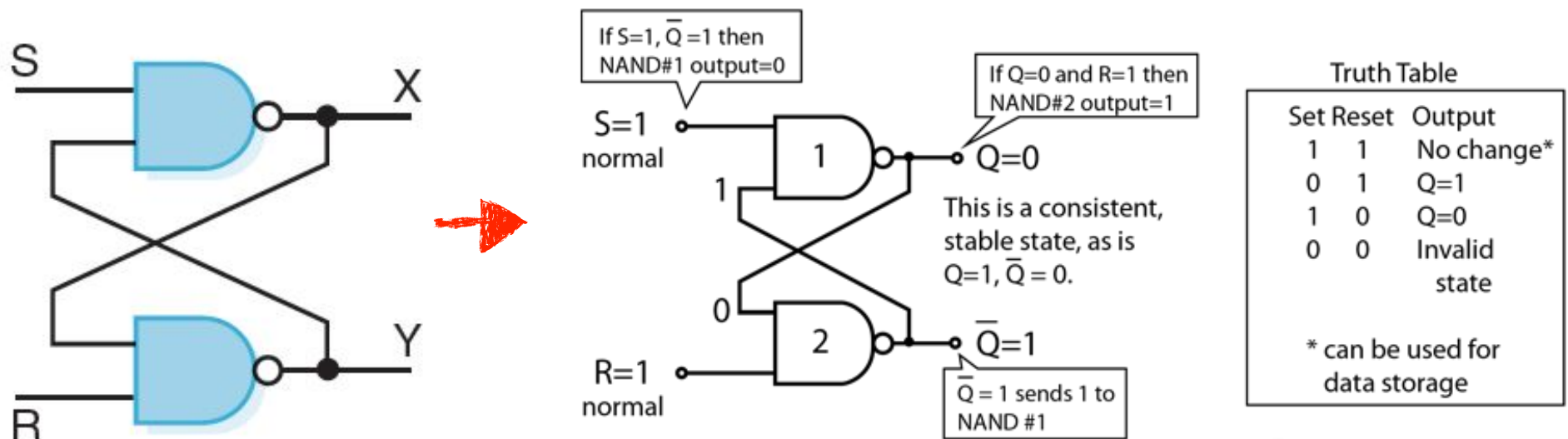


FIGURE 4.12 An S-R latch

How do we store the information?